



CIRCUIT BUILDER LAB

DIRECTIONS:

1. Draw a series circuit and label the parts. Parts include: a power source, a pathway, and a load. To help you identify these parts, definitions of each have been listed below.

Power source: A power source provides power.

Pathway: A pathway allows electricity to travel.

Load: A load is a user of electricity.





DIRECTIONS:

1. Draw a parallel circuit and label the parts. Parts include: a power source, a pathway, and a load. To help you identify these parts, definitions of each have been listed below.

Power source: A power source provides power.

Pathway: A pathway allows electricity to travel.

Load: A load is a user of electricity.

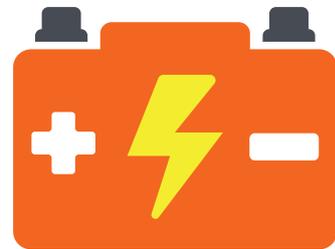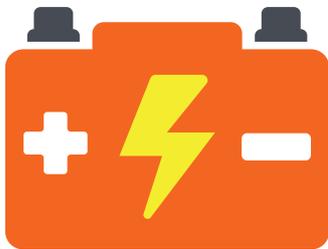

2. What do you observe about a parallel circuit?

3. If a lightbulb or load in a parallel circuit breaks, what happens to the parallel circuit? Explain why this happens.

4. Considering what you've learned about a parallel circuit, give an example of a parallel circuit found in your home or classroom.

DIRECTIONS:



1. Draw a switch circuit and label the parts. Parts include: a power source, a pathway, a switch, and a load. To help you identify these parts, definitions of each have been listed below.

Power source: A power source provides power.

Pathway: A pathway allows electricity to travel.

Load: A load is a user of electricity.

Switch: Component that can open or close the pathway.

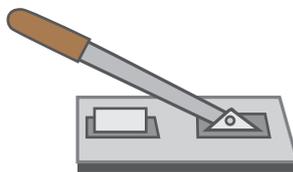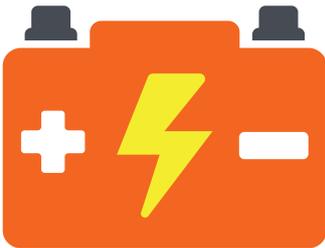

PART 4: CONDUCTOR OR INSULATOR

DIRECTIONS:

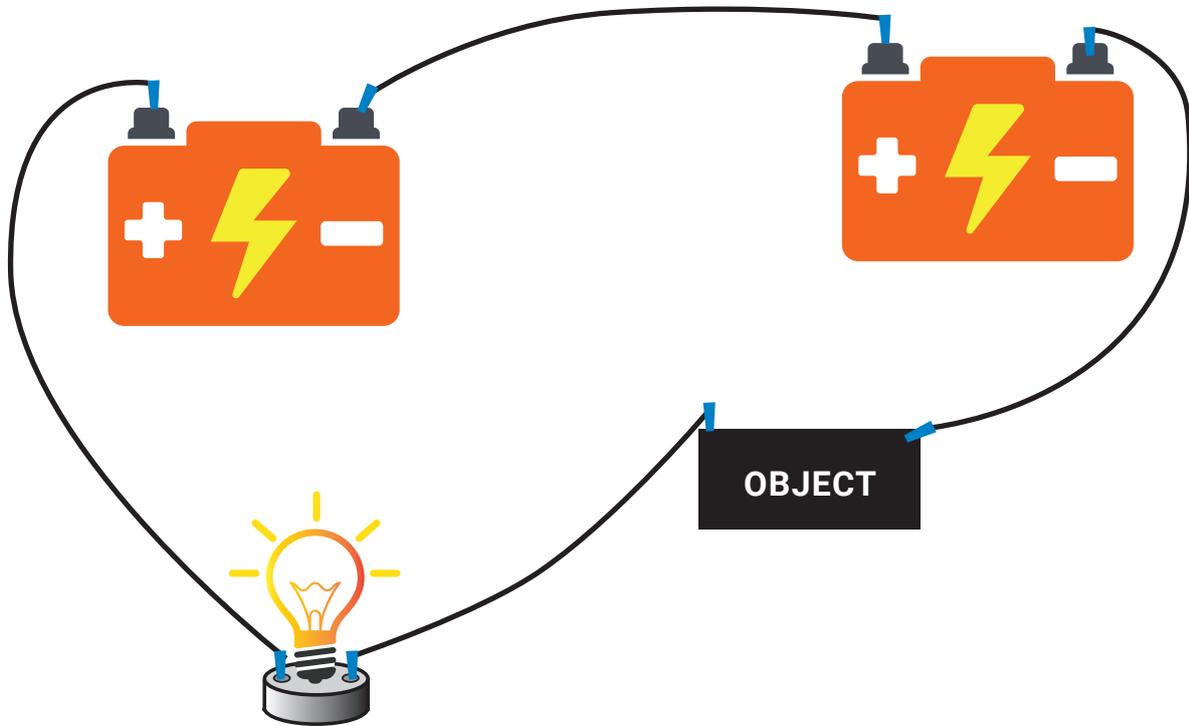
1. **CONNECTING THE BATTERIES LAST,**
work as a team to build your circuit to look like the picture below.
2. Test the items in your bag to see if they are conductors or insulators.



A **conductor** is a material that allows electricity to move through it easily.



An **insulator** is a material that DOES NOT allow electricity to move through it easily.



Object	Type of material (wood, metal, plastic, etc)	Prediction (conductor or insulator)	Result (conductor or insulator)

3. Classify your tested objects as conductors and insulators.



CONDUCTORS

What objects allowed the electrical energy to pass through?



INSULATORS

What objects DID NOT allow the electrical energy to pass through?

4. Based on your observations, circle the materials that are conductors of electricity.

Glass

Metal

Wood

Ceramic

Plastic

Copper

Water

Aluminum

Rubber

Diamonds

Silver

5. With water being a conductor, are YOU a conductor or insulator of electrical energy?